

EECS 168 Lab 4.1

Michael O'Dea

862066396

Session 21

modea

mode001

Lab 4, Week 1 CheckOff Video: Simulation result of example counter, The result of gate-level for 4-bit full adder, fa\_4bit\_synthesized.v, Final layout in Fig 49 for 4-bit full adder:

<https://drive.google.com/file/d/1Gfcjyek2pv3z3xdi0ATqr1SYgyYxOCKm/view?usp=sharing>

### Summary

\_\_\_\_\_In this part of the lab, I gained experience using Synopsys Design Compiler (DC) to perform hardware synthesis. A synthesis tool takes an RTL hardware description and a standard cell library as input and produces a gate level netlist as output. The resulting gate-level netlist is a completely structural description with standard cells only at the leaves of the design. I also gained experience transforming a gate-level netlist into a placed and routed layout using Synopsys IC Compiler (ICC). ICC takes a synthesized gate-level netlist and a standard cell library as input, then produces layout as an output. This was done with my 4 bit full adder.

Simulation result of example counter:




```

Contains Synopsys proprietary information.
Compiler version K-2015.09-SP1-1; Runtime version K-2015.09-SP1-1; Mar  1 17:57
2022
time=    0 ns, clk=0, reset=0, out=xxxx
time=   10 ns, clk=1, reset=0, out=xxxx
time=   11 ns, clk=1, reset=1, out=xxxx
time=   20 ns, clk=0, reset=1, out=xxxx
time=   30 ns, clk=1, reset=1, out=xxxx
time=   31 ns, clk=1, reset=0, out=0000
time=   40 ns, clk=0, reset=0, out=0000
time=   50 ns, clk=1, reset=0, out=0000
time=   51 ns, clk=1, reset=0, out=0001
time=   60 ns, clk=0, reset=0, out=0001
time=   70 ns, clk=1, reset=0, out=0001
time=   71 ns, clk=1, reset=0, out=0010
time=   80 ns, clk=0, reset=0, out=0010
time=   90 ns, clk=1, reset=0, out=0010
time=   91 ns, clk=1, reset=0, out=0011
time=  100 ns, clk=0, reset=0, out=0011
time=  110 ns, clk=1, reset=0, out=0011
time=  111 ns, clk=1, reset=0, out=0100
time=  120 ns, clk=0, reset=0, out=0100
time=  130 ns, clk=1, reset=0, out=0100
time=  131 ns, clk=1, reset=0, out=0101
time=  140 ns, clk=0, reset=0, out=0101
time=  150 ns, clk=1, reset=0, out=0101
time=  151 ns, clk=1, reset=0, out=0110
time=  160 ns, clk=0, reset=0, out=0110
time=  170 ns, clk=1, reset=0, out=0110
All tests completed sucessfully


$finish called from file "counter_tb.v", line 55.
$finish at simulation time 171.0 ns
      V C S   S i m u l a t i o n   R e p o r t
Time: 171000 ps
CPU Time:      0.300 seconds;      Data structure size:  0.0Mb
Tue Mar  1 17:57:42 2022
bender /home/cemaj/modea/eecs168/lab4-rtl/counter $ \

```

   The result of gate-level for 4-bit full adder:



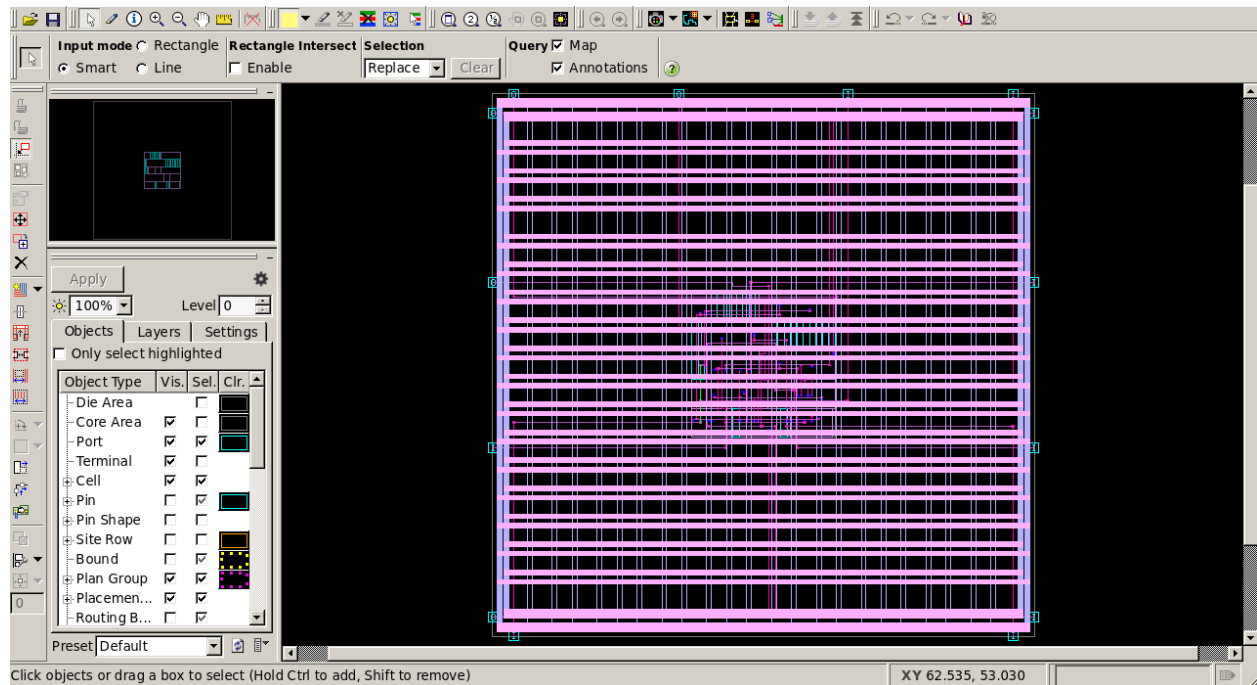Final layout in Fig 49 for 4-bit full adder:



## Issues

The only issue that I had in this lab was trying to view my synthesized 4 bit full adder. It wouldn't output and display the schematic even though I had no errors in setting it up after multiple tries. My final layout also differs from the example, but this is most likely the case of my 4 bit adder being different from the example setup one in lab 3. Other than that this lab was fine and I was able to run it without errors.

